

Loop and Cut Set

Dr. Tushar Sandhan

IITK, EE Department



- Let \mathcal{G} be a connected graph and T a subgraph of \mathcal{G} . We say that T is a **tree** of the connected graph \mathcal{G} if
 - 1 T is a connected subgraph.
 - 2 It contains all the nodes of \mathcal{G} .
 - 3 It contains no loops.

Tree

- Let \mathcal{G} be a connected graph and T a subgraph of \mathcal{G} . We say that T is a **tree** of the connected graph \mathcal{G} if
 - T is a connected subgraph.
 - It contains all the nodes of \mathcal{G} .
 - It contains no loops.
- Given a connected graph \mathcal{G} and a tree T , the branches of T are called **tree branches**, and the branches of \mathcal{G} not in T are called **links**.

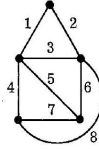


Figure 1: Planar graph G

Examples of trees of graph G .

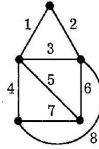


Figure 1: Planar graph G

Examples of trees of graph G .

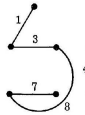


Figure 2: Tree T_1

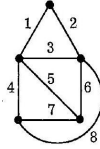


Figure 1: Planar graph G

Examples of trees of graph G .

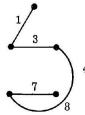


Figure 2: Tree T_1

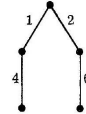


Figure 3: Tree T_2

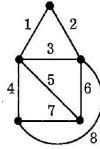


Figure 1: Planar graph G

Examples of trees of graph G .

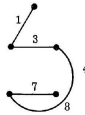


Figure 2: Tree T_1

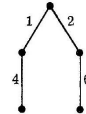


Figure 3: Tree T_2

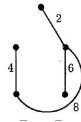


Figure 4: Tree T_3

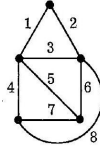


Figure 1: Planar graph G

Examples of trees of graph G .

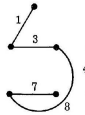


Figure 2: Tree T_1

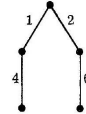


Figure 3: Tree T_2

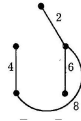


Figure 4: Tree T_3

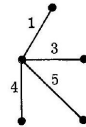


Figure 5: Tree T_4

Exercise

Draw all possible trees for the graph shown.

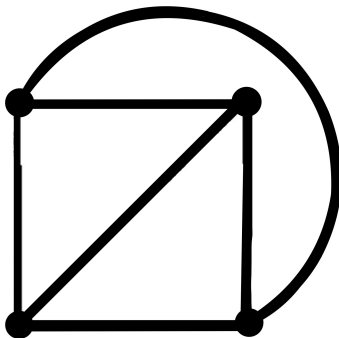


Figure 6: A connected graph with four nodes and six branches.

Fundamental theorem of graph theory

Given a connected graph \mathcal{G} of n_t nodes and b branches, and a tree T of \mathcal{G} . There is a unique path along the tree between any pair of nodes.

- There are $n_t - 1$ tree branches and $b - n_t + 1$ links.

Fundamental theorem of graph theory

Given a connected graph \mathcal{G} of n_t nodes and b branches, and a tree T of \mathcal{G} . There is a unique path along the tree between any pair of nodes.

- 1 There are $n_t - 1$ tree branches and $b - n_t + 1$ links.
- 2 Every link of T and the unique tree path between its nodes constitute a unique loop (this is called the **fundamental loop** associated with the link).

Fundamental theorem of graph theory

Given a connected graph \mathcal{G} of n_t nodes and b branches, and a tree T of \mathcal{G} . There is a unique path along the tree between any pair of nodes.

- 1 There are $n_t - 1$ tree branches and $b - n_t + 1$ links.
- 2 Every link of T and the unique tree path between its nodes constitute a unique loop (this is called the **fundamental loop** associated with the link).
- 3 Every tree branch of T together with some links defines a unique cut set of \mathcal{G} . This cut set is called a **fundamental cut set** associated with the tree branch.

Examples of subgraphs of \mathcal{G} in Fig.1 which are not trees.

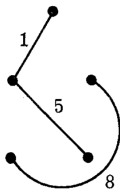


Figure 7: Subgraph 1

Violates property 1

Examples of subgraphs of \mathcal{G} in Fig.1 which are not trees.

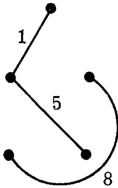


Figure 7: Subgraph 1

Violates property 1

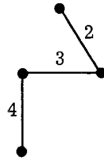


Figure 8: Subgraph 2

Violates property 2

Examples of subgraphs of \mathcal{G} in Fig.1 which are not trees.

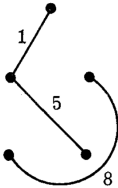


Figure 7: Subgraph 1

Violates property 1

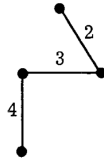


Figure 8: Subgraph 2

Violates property 2

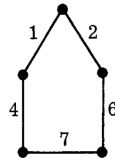


Figure 9: Subgraph 3

Violates property 3

- The theorem can readily be extended to the case in which the graph consists of several separate parts, as shown in the following statement.

- The theorem can readily be extended to the case in which the graph consists of several separate parts, as shown in the following statement.
- Suppose that \mathcal{G} has n_t nodes, b branches, and s separate parts. Let T_1, T_2, \dots, T_s be trees of each separate part, respectively. The set $\{T_1, T_2, \dots, T_s\}$ is called a forest of \mathcal{G} . Then the forest has $n_t - s$ branches, G has $b - n_t + s$ links, and the remaining statements of the theorem are true.

Loop analysis

- Consider a connected graph with b branches and n_t nodes. Pick an arbitrary tree T .

Loop analysis

- Consider a connected graph with b branches and n_t nodes. Pick an arbitrary tree T .
- There are $n = n_t - 1$ tree branches and $l = b - n$ links.

Loop analysis

- Consider a connected graph with b branches and n_t nodes. Pick an arbitrary tree T .
- There are $n = n_t - 1$ tree branches and $l = b - n$ links.
- Number the branches as follows: links first from 1 to l , tree branches next from $l + 1$ to b . Every link defines a fundamental loop.

Loop analysis

- Consider a connected graph with b branches and n_t nodes. Pick an arbitrary tree T .
- There are $n = n_t - 1$ tree branches and $l = b - n$ links.
- Number the branches as follows: links first from 1 to l , tree branches next from $l + 1$ to b . Every link defines a fundamental loop.

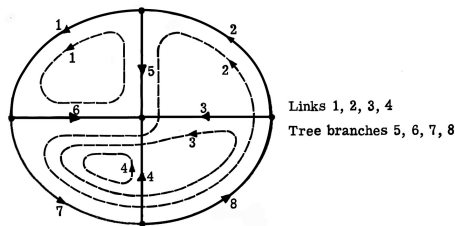


Figure 10: Fundamental loops for the chosen tree of a graph.

- The KVL equations can be written for the four fundamental loops in terms of the branch voltage from the above figure as follows:

Loop 1: $v_1 - v_5 + v_6 = 0$

Loop 2: $v_2 + v_5 - v_6 + v_7 + v_8 = 0$

Loop 3: $v_3 - v_6 + v_7 + v_8 = 0$

Loop 4: $v_4 - v_6 + v_7 = 0$

- The KVL equations can be written for the four fundamental loops in terms of the branch voltage from the above figure as follows:

Loop 1: $v_1 - v_5 + v_6 = 0$

Loop 2: $v_2 + v_5 - v_6 + v_7 + v_8 = 0$

Loop 3: $v_3 - v_6 + v_7 + v_8 = 0$

Loop 4: $v_4 - v_6 + v_7 = 0$

- In matrix form, the equation gives

$$l \text{ loops} \left\{ \begin{array}{c|c} \begin{bmatrix} 1 & 0 & 0 & 0 & -1 & 1 & 0 & 0 \\ 0 & 1 & 0 & 0 & 1 & -1 & 1 & 1 \\ 0 & 0 & 1 & 0 & 0 & -1 & 1 & 1 \\ 0 & 0 & 0 & 1 & 0 & -1 & 1 & 0 \end{bmatrix} & \begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \\ v_7 \\ v_8 \end{bmatrix} \end{array} \right. = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$\underbrace{\hspace{10em}}_{l \text{ links}} \qquad \underbrace{\hspace{10em}}_{n \text{ tree branches}}$

The first basic fact of loop analysis is as follows :

- The l linear homogeneous algebraic equations in v_1, \dots, v_b obtained by applying *KVL* to each fundamental loop constitute a set of l linearly independent equations.

The first basic fact of loop analysis is as follows :

- The l linear homogeneous algebraic equations in v_1, \dots, v_b obtained by applying *KVL* to each fundamental loop constitute a set of l linearly independent equations.
- The system of equations obtained from KVL is of the form

$$\mathbf{B}\mathbf{v} = \mathbf{0} \quad (1)$$

where \mathbf{B} is an $l \times b$ matrix called the fundamental loop matrix.

The first basic fact of loop analysis is as follows :

- The l linear homogeneous algebraic equations in v_1, \dots, v_b obtained by applying KVL to each fundamental loop constitute a set of l linearly independent equations.
- The system of equations obtained from KVL is of the form

$$\mathbf{B}\mathbf{v} = \mathbf{0} \quad (1)$$

where \mathbf{B} is an $l \times b$ matrix called the fundamental loop matrix.

- Furthermore, its (i, k) th element is defined as follows:

$$b_{ik} = \begin{cases} 1 & \text{if branch } k \text{ is in loop } i \text{ and their reference directions agree} \\ -1 & \text{if branch } k \text{ is in loop } i \text{ and their reference directions do not} \\ & \text{agree} \\ 0 & \text{if branch } k \text{ is not in loop } i \end{cases}$$

- Each fundamental loop includes one link only and since the orientations of the loop and the link are picked to be the same, it is clear that if we number the links $1, 2, \dots, l$ and the tree branches $l + 1, l + 2, \dots, b$, the matrix **B** has the form

$$\mathbf{B} = \left[\begin{array}{c|c} \underbrace{\mathbf{1}_l}_{l \text{ links}} & \underbrace{\mathbf{F}}_{n \text{ tree branches}} \end{array} \right] \} l \text{ loops} \quad (2)$$

where $\mathbf{1}_l$ designates a unit matrix of order l and **F** designates a rectangular matrix of l rows and n columns.

- Each fundamental loop includes one link only and since the orientations of the loop and the link are picked to be the same, it is clear that if we number the links $1, 2, \dots, l$ and the tree branches $l + 1, l + 2, \dots, b$, the matrix \mathbf{B} has the form

$$\mathbf{B} = \left[\begin{array}{c|c} \underbrace{\mathbf{1}_l}_{l \text{ links}} & \underbrace{\mathbf{F}}_{n \text{ tree branches}} \end{array} \right] \} l \text{ loops} \quad (2)$$

where $\mathbf{1}_l$ designates a unit matrix of order l and \mathbf{F} designates a rectangular matrix of l rows and n columns.

- We have established the fact that the l fundamental loop equations written in terms of the branch voltages constitute a set of l linearly independent equations.

The second basic fact of loop analysis is as follows :

- Let i_1, i_2, \dots, i_l the currents in the l links of the tree T . Each tree branch current is the superposition of one or more loop currents. So,

$$\mathbf{j} = \mathbf{B}^T \mathbf{i} \quad (3)$$

where \mathbf{B}^T is the transpose of the fundamental loop matrix.

Example

Let us consider our example of Fig. 10. We can write the following equations :

$$j_1 = i_1$$

$$j_2 = i_2$$

$$j_3 = i_3$$

$$j_4 = i_4$$

$$j_5 = -i_1 + i_2$$

$$j_6 = i_1 - i_2 - i_3 - i_4$$

$$j_7 = i_2 + i_3 + i_4$$

$$j_8 = i_2 + i_3$$

In matrix form the equation is

$$\begin{bmatrix} \dot{j}_1 \\ \dot{j}_2 \\ \dot{j}_3 \\ \dot{j}_4 \\ \dot{j}_5 \\ \dot{j}_6 \\ \dot{j}_7 \\ \dot{j}_8 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \\ -1 & 1 & 0 & 0 \\ 1 & -1 & -1 & -1 \\ 0 & 1 & 1 & 1 \\ 0 & 1 & 1 & 0 \end{bmatrix} \begin{bmatrix} \dot{i}_1 \\ \dot{i}_2 \\ \dot{i}_3 \\ \dot{i}_4 \end{bmatrix}$$

Loop analysis for LTI networks

- The branch equations are written in matrix form as follows:

$$\mathbf{v} = \mathbf{R}\mathbf{j} + \mathbf{v}_s - \mathbf{R}\mathbf{j}_s \quad (4)$$

Loop analysis for LTI networks

- The branch equations are written in matrix form as follows:

$$\mathbf{v} = \mathbf{R}\mathbf{j} + \mathbf{v}_s - \mathbf{R}\mathbf{j}_s \quad (4)$$

- As before, \mathbf{R} is a diagonal branch resistance matrix of dimension b , and \mathbf{v}_s and \mathbf{j}_s are voltage source and current source vectors, respectively.

Loop analysis for LTI networks

- The branch equations are written in matrix form as follows:

$$\mathbf{v} = \mathbf{R}\mathbf{j} + \mathbf{v}_s - \mathbf{R}\mathbf{j}_s \quad (4)$$

- As before, \mathbf{R} is a diagonal branch resistance matrix of dimension b , and \mathbf{v}_s and \mathbf{j}_s are voltage source and current source vectors, respectively.
- Combining Eqs.(1), (3), and(4), we obtain

$$\mathbf{B}\mathbf{R}\mathbf{B}^T\mathbf{i} = -\mathbf{B}\mathbf{v}_s + \mathbf{B}\mathbf{R}\mathbf{j}_s \quad (5)$$

Loop analysis for LTI networks

- The branch equations are written in matrix form as follows:

$$\mathbf{v} = \mathbf{R}\mathbf{j} + \mathbf{v}_s - \mathbf{R}\mathbf{j}_s \quad (4)$$

- As before, \mathbf{R} is a diagonal branch resistance matrix of dimension b , and \mathbf{v}_s and \mathbf{j}_s are voltage source and current source vectors, respectively.
- Combining Eqs.(1), (3), and(4), we obtain

$$\mathbf{B}\mathbf{R}\mathbf{B}^T\mathbf{i} = -\mathbf{B}\mathbf{v}_s + \mathbf{B}\mathbf{R}\mathbf{j}_s \quad (5)$$

or

$$\mathbf{Z}_l\mathbf{i} = \mathbf{e}_s \quad (6)$$

Loop analysis for LTI networks

- The branch equations are written in matrix form as follows:

$$\mathbf{v} = \mathbf{R}\mathbf{j} + \mathbf{v}_s - \mathbf{R}\mathbf{j}_s \quad (4)$$

- As before, \mathbf{R} is a diagonal branch resistance matrix of dimension b , and \mathbf{v}_s and \mathbf{j}_s are voltage source and current source vectors, respectively.
- Combining Eqs.(1), (3), and(4), we obtain

$$\mathbf{B}\mathbf{R}\mathbf{B}^T\mathbf{i} = -\mathbf{B}\mathbf{v}_s + \mathbf{B}\mathbf{R}\mathbf{j}_s \quad (5)$$

or

$$\mathbf{Z}_l\mathbf{i} = \mathbf{e}_s \quad (6)$$

where

$$\mathbf{Z}_l \triangleq \mathbf{B}\mathbf{R}\mathbf{B}^T \quad (7)$$

$$\mathbf{e}_s \triangleq -\mathbf{B}\mathbf{v}_s + \mathbf{B}\mathbf{R}\mathbf{j}_s \quad (8)$$

- \mathbf{Z}_l is called the loop impedance matrix of order l , and \mathbf{e}_s is the loop voltage source vector.

- \mathbf{Z}_l is called the loop impedance matrix of order l , and \mathbf{e}_s is the loop voltage source vector.
- The loop impedance matrix has properties similar to those of the mesh impedance matrix discussed in the previous lecture.

- \mathbf{Z}_l is called the loop impedance matrix of order l , and \mathbf{e}_s is the loop voltage source vector.
- The loop impedance matrix has properties similar to those of the mesh impedance matrix discussed in the previous lecture.
- The matrix \mathbf{Z}_l is symmetric.

- \mathbf{Z}_l is called the loop impedance matrix of order l , and \mathbf{e}_s is the loop voltage source vector.
- The loop impedance matrix has properties similar to those of the mesh impedance matrix discussed in the previous lecture.
- The matrix \mathbf{Z}_l is symmetric.
- Let us rewrite Eq. 6 as follows:

$$\begin{bmatrix} z_{11} & z_{12} & \dots & z_{1l} \\ z_{21} & z_{22} & \dots & z_{2l} \\ \dots & \dots & \dots & \cdot \\ z_{l1} & z_{l2} & \dots & z_{ll} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ \vdots \\ i_l \end{bmatrix} = \begin{bmatrix} e_{s1} \\ e_{s2} \\ \vdots \\ e_{sl} \end{bmatrix}$$

Example

Let us consider the network of below . The graph of the network is that of Fig. 10.

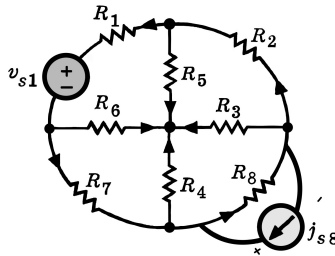


Figure 11: Example of loop analysis.

The branch equation is

$$\begin{bmatrix} v_1 \\ v_2 \\ v_3 \\ v_4 \\ v_5 \\ v_6 \\ v_7 \\ v_8 \end{bmatrix} = \begin{bmatrix} R_1 & & & & & & & \\ & R_2 & & & & & & \\ & & R_3 & & & & & \\ & & & R_4 & & & & \\ & & & & R_5 & & & \\ & & & & & R_6 & & \\ & & & & & & R_7 & \\ & & & & & & & R_8 \end{bmatrix} \begin{bmatrix} j_1 \\ j_2 \\ j_3 \\ j_4 \\ j_5 \\ j_6 \\ j_7 \\ j_8 \end{bmatrix} + \begin{bmatrix} v_{s1} \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ R_8 j_{s8} \end{bmatrix}$$

Using Eq. 7, we can obtain the loop impedance matrix

$$\mathbf{Z}_l = \mathbf{B}\mathbf{R}\mathbf{B}^T$$

$$= \begin{bmatrix} R_1 + R_5 + R_6 & -R_5 - R_6 & -R_6 & -R_6 \\ -R_5 - R_6 & R_2 + R_5 + R_6 + R_7 + R_8 & R_6 + R_7 + R_8 & R_6 + R_7 \\ -R_6 & R_6 + R_7 + R_8 & R_3 + R_6 + R_7 + R_8 & R_6 + R_7 \\ -R_6 & R_6 + R_7 & R_6 + R_7 & R_4 + R_6 + R_7 \end{bmatrix}$$

Using Eq. 7, we can obtain the loop impedance matrix

$$\mathbf{Z}_l = \mathbf{B}\mathbf{R}\mathbf{B}^T$$

$$= \begin{bmatrix} R_1 + R_5 + R_6 & -R_5 - R_6 & -R_6 & -R_6 \\ -R_5 - R_6 & R_2 + R_5 + R_6 + R_7 + R_8 & R_6 + R_7 + R_8 & R_6 + R_7 \\ -R_6 & R_6 + R_7 + R_8 & R_3 + R_6 + R_7 + R_8 & R_6 + R_7 \\ -R_6 & R_6 + R_7 & R_6 + R_7 & R_4 + R_6 + R_7 \end{bmatrix}$$

The loop equations are

$$\begin{bmatrix} R_1 + R_5 + R_6 & -R_5 - R_6 & -R_6 & -R_6 \\ -R_5 - R_6 & R_2 + R_5 + R_6 + R_7 + R_8 & R_6 + R_7 + R_8 & R_6 + R_7 \\ -R_6 & R_6 + R_7 + R_8 & R_3 + R_6 + R_7 + R_8 & R_6 + R_7 \\ -R_6 & R_6 + R_7 & R_6 + R_7 & R_4 + R_6 + R_7 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} -v_{s1} \\ -R_8 j_{s8} \\ -R_8 j_{s8} \\ 0 \end{bmatrix}$$

Properties of the Loop impedance matrix

The following properties of the loop impedance matrix $\mathbf{Z}_l(j\omega)$ follow from the relation

$$\mathbf{Z}_l(j\omega) = \mathbf{B}\mathbf{Z}_b(j\omega)\mathbf{B}^T \quad (9)$$

Properties of the Loop impedance matrix

The following properties of the loop impedance matrix $\mathbf{Z}_l(j\omega)$ follow from the relation

$$\mathbf{Z}_l(j\omega) = \mathbf{B}\mathbf{Z}_b(j\omega)\mathbf{B}^T \quad (9)$$

- If the network has no coupling elements, the branch impedance matrix $\mathbf{Z}_b(j\omega)$ is diagonal, and the loop impedance matrix $\mathbf{Z}_l(j\omega)$ is symmetric.

Properties of the Loop impedance matrix

The following properties of the loop impedance matrix $\mathbf{Z}_l(j\omega)$ follow from the relation

$$\mathbf{Z}_l(j\omega) = \mathbf{B}\mathbf{Z}_b(j\omega)\mathbf{B}^T \quad (9)$$

- 1 If the network has no coupling elements, the branch impedance matrix $\mathbf{Z}_b(j\omega)$ is diagonal, and the loop impedance matrix $\mathbf{Z}_l(j\omega)$ is symmetric.
- 2 Also, if the network has no coupling elements, the loop impedance matrix $\mathbf{Z}_l(j\omega)$ can be written by inspection.
 - The i th diagonal element of $\mathbf{Z}_l(j\omega)$, z_{ii} , is equal to the sum of the impedances in loop i ; z_{ii} is called the self-impedance of loop i .

Properties of the Loop impedance matrix

The following properties of the loop impedance matrix $\mathbf{Z}_l(j\omega)$ follow from the relation

$$\mathbf{Z}_l(j\omega) = \mathbf{B}\mathbf{Z}_b(j\omega)\mathbf{B}^T \quad (9)$$

- 1 If the network has no coupling elements, the branch impedance matrix $\mathbf{Z}_b(j\omega)$ is diagonal, and the loop impedance matrix $\mathbf{Z}_l(j\omega)$ is symmetric.
- 2 Also, if the network has no coupling elements, the loop impedance matrix $\mathbf{Z}_l(j\omega)$ can be written by inspection.
 - The i th diagonal element of $\mathbf{Z}_l(j\omega)$, z_{ii} , is equal to the sum of the impedances in loop i ; z_{ii} is called the self-impedance of loop i .
 - The (i, k) element of $\mathbf{Z}_l(j\omega)$, z_{ik} , is equal to plus or minus the sum of the impedances of the branches common to loop i and to loop k ; the plus sign applies if, in the branches common to loop i and loop k , the loop reference directions agree, and the minus sign applies when they are opposite.

- If all current sources are converted, by Thévenin's theorem, into voltage sources, then the forcing term e_{si} is the algebraic sum of all the source voltages in loop i : the voltage sources whose reference direction pushes the current in the i th loop reference direction are assigned a positive sign, the others a negative sign.

- 1 If all current sources are converted, by Thévenin's theorem, into voltage sources, then the forcing term e_{si} is the algebraic sum of all the source voltages in loop i : the voltage sources whose reference direction pushes the current in the i th loop reference direction are assigned a positive sign, the others a negative sign.
- 2 If the network is resistive and if all its resistances are positive, then $\det(\mathbf{Z}_I) > 0$.

Cut set analysis

- Cut-set analysis is the dual of loop analysis.

Cut set analysis

- Cut-set analysis is the dual of loop analysis.
- First, pick a tree; call it T . Next we number branches; as before, the links range from 1 to l , and the tree branches range from $l + 1$ to b .

Cut set analysis

- Cut-set analysis is the dual of loop analysis.
- First, pick a tree; call it T . Next we number branches; as before, the links range from 1 to l , and the tree branches range from $l + 1$ to b .
- We know that every tree branch defines (for the given tree) a unique fundamental cut set.

Cut set analysis

- Cut-set analysis is the dual of loop analysis.
- First, pick a tree; call it T . Next we number branches; as before, the links range from 1 to l , and the tree branches range from $l + 1$ to b .
- We know that every tree branch defines (for the given tree) a unique fundamental cut set.
- That cut set is made up of links and of one tree branch, namely the tree branch which defines the cut set.

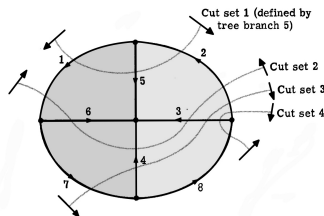


Figure 12: Fundamental cut sets for the chosen tree of a given graph.

- Let us number the cut sets as follows: cut set 1 is associated with tree branch 5 , cut set 2 with tree branch 6 , etc.

- Let us number the cut sets as follows: cut set 1 is associated with tree branch 5 , cut set 2 with tree branch 6 , etc.
- If we apply KCL to the four cut sets, we obtain
 - Cut set 1: $j_1 - j_2 + j_5 = 0$
 - Cut set 2: $-j_1 + j_2 + j_3 + j_4 + j_6 = 0$
 - Cut set 3: $-j_2 - j_3 - j_4 + j_7 = 0$
 - Cut set 4: $-j_2 - j_3 + j_8 = 0$

- Let us number the cut sets as follows: cut set 1 is associated with tree branch 5 , cut set 2 with tree branch 6 , etc.
- If we apply KCL to the four cut sets, we obtain
 Cut set 1: $j_1 - j_2 + j_5 = 0$
 Cut set 2: $-j_1 + j_2 + j_3 + j_4 + j_6 = 0$
 Cut set 3: $-j_2 - j_3 - j_4 + j_7 = 0$
 Cut set 4: $-j_2 - j_3 + j_8 = 0$
- In matrix form, the equation is

$$\begin{bmatrix} 1 & -1 & 0 & 0 & 1 & 0 & 0 & 0 \\ -1 & 1 & 1 & 1 & 0 & 1 & 0 & 0 \\ 0 & -1 & -1 & -1 & 0 & 0 & 1 & 0 \\ 0 & -1 & -1 & 0 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} j_1 \\ j_2 \\ j_3 \\ j_4 \\ j_5 \\ j_6 \\ j_7 \\ j_8 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

The first basic fact of cut-set analysis is as follows:

- In general, if we apply KCL to each one of the n fundamental cut sets, we obtain a system of n linear homogeneous equations in b unknowns j_1, j_2, \dots, j_b .

The first basic fact of cut-set analysis is as follows:

- In general, if we apply KCL to each one of the n fundamental cut sets, we obtain a system of n linear homogeneous equations in b unknowns j_1, j_2, \dots, j_b .
- The KCL equations are of the form

$$\mathbf{Qj} = \mathbf{0} \quad (10)$$

The first basic fact of cut-set analysis is as follows:

- In general, if we apply KCL to each one of the n fundamental cut sets, we obtain a system of n linear homogeneous equations in b unknowns j_1, j_2, \dots, j_b .
- The KCL equations are of the form

$$\mathbf{Q}\mathbf{j} = \mathbf{0} \quad (10)$$

where \mathbf{Q} is an $n \times b$ matrix defined by

$$q_{ik} = \begin{cases} 1 & \text{if branch } k \text{ belongs to cut set } (i) \text{ and has the same reference direction} \\ -1 & \text{if branch } k \text{ belongs to cut set } (i) \text{ and has the opposite reference direction} \\ 0 & \text{if branch } k \text{ does not belong to cut set } (i) \end{cases} \quad (11)$$

- $\mathbf{Q} = [q_{ik}]$ is called the fundamental cut-set matrix. As before we note that it is of the form

$$\mathbf{Q} = \left[\begin{array}{c|c} \mathbf{E} & \mathbf{I}_n \\ \hline \underbrace{\phantom{\mathbf{E}}}_{l \text{ links}} & \underbrace{\phantom{\mathbf{I}_n}}_{n \text{ tree branches}} \end{array} \right] \left. \vphantom{\begin{array}{c|c} \mathbf{E} & \mathbf{I}_n \end{array}} \right\} n \text{ cut sets} \quad (12)$$

where \mathbf{E} is an appropriate $n \times l$ matrix with elements $-1, +1, 0$, and \mathbf{I}_n is the $n \times n$ unit matrix.

- $\mathbf{Q} = [q_{ik}]$ is called the fundamental cut-set matrix. As before we note that it is of the form

$$\mathbf{Q} = \left[\begin{array}{c|c} \mathbf{E} & \mathbf{I}_n \\ \hline \underbrace{\phantom{\mathbf{E}}}_{l \text{ links}} & \underbrace{\phantom{\mathbf{I}_n}}_{n \text{ tree branches}} \end{array} \right] \left. \vphantom{\begin{array}{c|c} \mathbf{E} & \mathbf{I}_n \end{array}} \right\} n \text{ cut sets} \quad (12)$$

where \mathbf{E} is an appropriate $n \times l$ matrix with elements $-1, +1, 0$, and \mathbf{I}_n is the $n \times n$ unit matrix.

- Obviously, \mathbf{Q} has a rank n since it includes the unit matrix \mathbf{I}_n .

- $\mathbf{Q} = [q_{ik}]$ is called the fundamental cut-set matrix. As before we note that it is of the form

$$\mathbf{Q} = \left[\begin{array}{c|c} \underbrace{\mathbf{E}}_{l \text{ links}} & \underbrace{\mathbf{I}_n}_{n \text{ tree branches}} \end{array} \right] \left. \vphantom{\begin{array}{c|c} \mathbf{E} & \mathbf{I}_n \end{array}} \right\} n \text{ cut sets} \quad (12)$$

where \mathbf{E} is an appropriate $n \times l$ matrix with elements $-1, +1, 0$, and \mathbf{I}_n is the $n \times n$ unit matrix.

- Obviously, \mathbf{Q} has a rank n since it includes the unit matrix \mathbf{I}_n .
- Hence, the n fundamental cut-set equations in terms of the branch currents are linearly independent.

The second basic fact of cut-set analysis is :

- Turning now to KVL, we note that each branch voltage can be expressed as a linear combination of the tree-branch voltages.

The second basic fact of cut-set analysis is :

- Turning now to KVL, we note that each branch voltage can be expressed as a linear combination of the tree-branch voltages.
- Let e_1, e_2, \dots, e_n be the tree-branch voltages. For the example in Fig. 12, from KVL we obtain the following equations:

$$v_1 = v_5 - v_6 = e_1 - e_2$$

$$v_2 = -v_5 + v_6 - v_7 - v_8 = -e_1 + e_2 - e_3 - e_4$$

$$v_3 = v_6 - v_7 - v_8 = e_2 - e_3 - e_4$$

$$v_4 = v_6 - v_7 = e_2 - e_3$$

$$v_5 = e_1$$

$$v_6 = e_2$$

$$v_7 = e_3$$

$$v_8 = e_4$$

The second basic fact of cut-set analysis is :

- Turning now to KVL, we note that each branch voltage can be expressed as a linear combination of the tree-branch voltages.
- Let e_1, e_2, \dots, e_n be the tree-branch voltages. For the example in Fig. 12, from KVL we obtain the following equations:

$$v_1 = v_5 - v_6 = e_1 - e_2$$

$$v_2 = -v_5 + v_6 - v_7 - v_8 = -e_1 + e_2 - e_3 - e_4$$

$$v_3 = v_6 - v_7 - v_8 = e_2 - e_3 - e_4$$

$$v_4 = v_6 - v_7 = e_2 - e_3$$

$$v_5 = e_1$$

$$v_6 = e_2$$

$$v_7 = e_3$$

$$v_8 = e_4$$

- By following the reasoning dual to that of the loop analysis,

$$\mathbf{v} = \mathbf{Q}^T \mathbf{e} \quad (13)$$

Cut-set analysis for LTI networks

- In cut-set analysis Kirchhoff's laws are expressed by $\mathbf{Qj} = \mathbf{0}$ and $\mathbf{v} = \mathbf{Q}^T \mathbf{e}$

Cut-set analysis for LTI networks

- In cut-set analysis Kirchhoff's laws are expressed by $\mathbf{Qj} = \mathbf{0}$ and $\mathbf{v} = \mathbf{Q}^T \mathbf{e}$
- These equations are combined with branch equations to form network equations with the n tree-branch voltages e_1, e_2, \dots, e_n as network variables.

Cut-set analysis for LTI networks

- In cut-set analysis Kirchhoff's laws are expressed by $\mathbf{Qj} = \mathbf{0}$ and $\mathbf{v} = \mathbf{Q}^T \mathbf{e}$
- These equations are combined with branch equations to form network equations with the n tree-branch voltages e_1, e_2, \dots, e_n as network variables.
- The branch equations are written in matrix form as follows:

$$\mathbf{j} = \mathbf{Gv} + \mathbf{j}_s - \mathbf{Gvv}_s \quad (14)$$

\mathbf{G} is the diagonal branch conductance matrix of dimension b and \mathbf{j}_s and \mathbf{v}_s are the source vectors.

Cut-set analysis for LTI networks

- In cut-set analysis Kirchhoff's laws are expressed by $\mathbf{Qj} = \mathbf{0}$ and $\mathbf{v} = \mathbf{Q}^T \mathbf{e}$
- These equations are combined with branch equations to form network equations with the n tree-branch voltages e_1, e_2, \dots, e_n as network variables.
- The branch equations are written in matrix form as follows:

$$\mathbf{j} = \mathbf{Gv} + \mathbf{j}_s - \mathbf{Gv}_s \quad (14)$$

\mathbf{G} is the diagonal branch conductance matrix of dimension b and \mathbf{j}_s and \mathbf{v}_s are the source vectors.

- Combining Eqs. 10, 13, and 14, we obtain

$$\mathbf{QGQ}^T \mathbf{e} = \mathbf{QGv}_s - \mathbf{Qj}_s \quad (15)$$

- Eq. 15 can also written as

$$\mathbf{Y}_q \mathbf{e} = \mathbf{i}_s \quad (16)$$

- Eq. 15 can also written as

$$\mathbf{Y}_q \mathbf{e} = \mathbf{i}_s \quad (16)$$

where

$$\mathbf{Y}_q \triangleq \mathbf{Q} \mathbf{G} \mathbf{Q}^T \quad \mathbf{i}_s \triangleq \mathbf{Q} \mathbf{G} \mathbf{v}_s - \mathbf{Q} \mathbf{j}_s \quad (17)$$

\mathbf{Y}_q is called the **cut-set admittance matrix**, and \mathbf{i}_s is the **cut-set current source vector**.

- Eq. 15 can also written as

$$\mathbf{Y}_q \mathbf{e} = \mathbf{i}_s \quad (16)$$

where

$$\mathbf{Y}_q \triangleq \mathbf{Q} \mathbf{G} \mathbf{Q}^T \quad \mathbf{i}_s \triangleq \mathbf{Q} \mathbf{G} \mathbf{v}_s - \mathbf{Q} \mathbf{j}_s \quad (17)$$

\mathbf{Y}_q is called the **cut-set admittance matrix**, and \mathbf{i}_s is the **cut-set current source vector**.

- In scalar form, the cut-set equations are

$$\begin{bmatrix} y_{11} & y_{12} & \cdots & y_{1n} \\ y_{21} & y_{22} & \cdots & y_{2n} \\ \cdots & \cdots & \cdots & \cdots \\ y_{n1} & y_{n2} & \cdots & y_{nn} \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ \vdots \\ e_n \end{bmatrix} = \begin{bmatrix} i_{s1} \\ i_{s2} \\ \vdots \\ i_{sn} \end{bmatrix}$$

Properties of the cut-set admittance matrix

The cut-set admittance matrix \mathbf{Y}_q has a number of properties based on the equation

$$\mathbf{Y}_q(j\omega) = \mathbf{Q}\mathbf{Y}_b(j\omega)\mathbf{Q}^T \quad (18)$$

Properties of the cut-set admittance matrix

The cut-set admittance matrix \mathbf{Y}_q has a number of properties based on the equation

$$\mathbf{Y}_q(j\omega) = \mathbf{Q}\mathbf{Y}_b(j\omega)\mathbf{Q}^T \quad (18)$$

- If the network has no coupling elements, the branch admittance matrix $\mathbf{Y}_b(j\omega)$ is diagonal, and $\mathbf{Y}_q(j\omega)$ is symmetric.

Properties of the cut-set admittance matrix

The cut-set admittance matrix \mathbf{Y}_q has a number of properties based on the equation

$$\mathbf{Y}_q(j\omega) = \mathbf{Q}\mathbf{Y}_b(j\omega)\mathbf{Q}^T \quad (18)$$

- 1 If the network has no coupling elements, the branch admittance matrix $\mathbf{Y}_b(j\omega)$ is diagonal, and $\mathbf{Y}_q(j\omega)$ is symmetric.
- 2 If there are no coupling elements,
 - The i th diagonal element of $\mathbf{Y}_q(j\omega)$, $y_{ii}(j\omega)$, is equal to the sum of the admittances of the branches of the i th cut set.

Properties of the cut-set admittance matrix

The cut-set admittance matrix \mathbf{Y}_q has a number of properties based on the equation

$$\mathbf{Y}_q(j\omega) = \mathbf{Q}\mathbf{Y}_b(j\omega)\mathbf{Q}^T \quad (18)$$

- 1 If the network has no coupling elements, the branch admittance matrix $\mathbf{Y}_b(j\omega)$ is diagonal, and $\mathbf{Y}_q(j\omega)$ is symmetric.
- 2 If there are no coupling elements,
 - The i th diagonal element of $\mathbf{Y}_q(j\omega)$, $y_{ii}(j\omega)$, is equal to the sum of the admittances of the branches of the i th cut set.
 - The (i, k) element of $\mathbf{Y}_q(j\omega)$, $y_{ik}(j\omega)$, is equal to the sum of all the admittances of branches common to cut set i and cut set k when, in the branches common to their two cut sets, their reference directions agree; otherwise, y_{ik} is the negative of that sum.

- If all the voltage sources are transformed to current sources, then i_{sk} is the algebraic sum of all current sources in cut set k : the current sources whose reference direction is opposite to that of the k th cut set reference direction are assigned a positive sign, all others are assigned a negative sign.

- 1 If all the voltage sources are transformed to current sources, then i_{sk} is the algebraic sum of all current sources in cut set k : the current sources whose reference direction is opposite to that of the k th cut set reference direction are assigned a positive sign, all others are assigned a negative sign.
- 2 If the network is resistive and if all branch resistances are positive, then $\det(\mathbf{Y}_q) > 0$.

Example

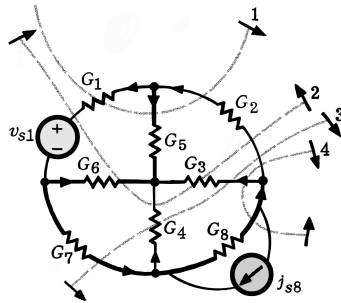


Figure 13: Example of cut-set analysis.

For the above network, the cut-set equations are

$$\begin{bmatrix} G_1 + G_2 + G_5 & -G_1 - G_2 & G_2 & G_2 \\ -G_1 - G_2 & G_1 + G_2 + G_3 + G_4 + G_6 & -G_2 - G_3 - G_4 & -G_2 - G_3 \\ G_2 & -G_2 - G_3 - G_4 & G_2 + G_3 + G_4 + G_7 & G_2 + G_3 \\ G_2 & -G_2 - G_3 & G_2 + G_3 & G_2 + G_3 + G_8 \end{bmatrix} \begin{bmatrix} e_1 \\ e_2 \\ e_3 \\ e_4 \end{bmatrix} = \begin{bmatrix} G_1 v_{s1} \\ -G_1 v_{s1} \\ 0 \\ j_{s3} \end{bmatrix}$$

Some comments on loop and cut set analysis

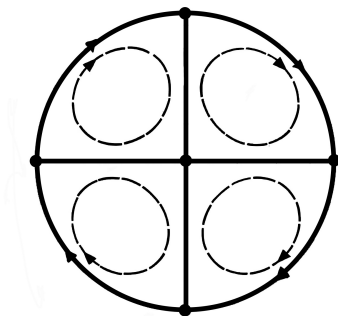


Figure 14: Fundamental loops for the chosen tree are identical with meshes.

Some comments on loop and cut set analysis

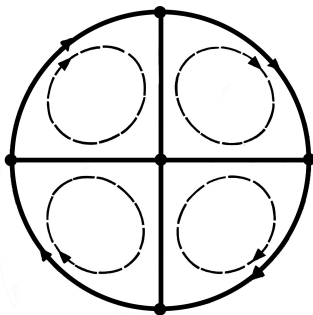


Figure 14: Fundamental loops for the chosen tree are identical with meshes.

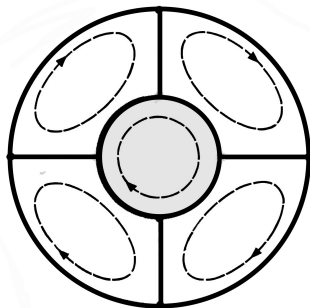


Figure 15: A graph showing that meshes are not special cases of fundamental loops.

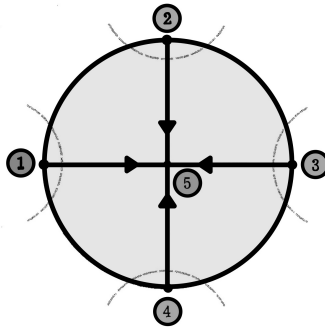


Figure 16: The four fundamental cut sets for the chosen tree coincide with the set of branches connected to nodes (1), (2), (3), and (4).

Relationship between B and Q

- **THEOREM** Call \mathbf{B} the fundamental loop matrix and \mathbf{Q} the fundamental cut-set matrix of the same oriented \mathcal{G} , and let both matrices pertain to the same tree T ; then

$$\mathbf{B}\mathbf{Q}^T = \mathbf{0} \text{ and } \mathbf{Q}\mathbf{B}^T = \mathbf{0} \quad (19)$$

Relationship between B and Q

- **THEOREM** Call \mathbf{B} the fundamental loop matrix and \mathbf{Q} the fundamental cut-set matrix of the same oriented \mathcal{G} , and let both matrices pertain to the same tree T ; then

$$\mathbf{B}\mathbf{Q}^T = \mathbf{0} \text{ and } \mathbf{Q}\mathbf{B}^T = \mathbf{0} \quad (19)$$

- If we number the links from 1 to l and number the tree branches from $l + 1$ to b , then

$$\mathbf{B} = \begin{bmatrix} \mathbf{1}_l & \mathbf{F} \end{bmatrix} \quad \text{and} \quad \mathbf{Q} = \begin{bmatrix} -\mathbf{F}^T & \mathbf{1}_n \end{bmatrix} \quad (20)$$

Relationship between B and Q

- **THEOREM** Call \mathbf{B} the fundamental loop matrix and \mathbf{Q} the fundamental cut-set matrix of the same oriented \mathcal{G} , and let both matrices pertain to the same tree T ; then

$$\mathbf{B}\mathbf{Q}^T = \mathbf{0} \text{ and } \mathbf{Q}\mathbf{B}^T = \mathbf{0} \quad (19)$$

- If we number the links from 1 to l and number the tree branches from $l+1$ to b , then

$$\mathbf{B} = \begin{bmatrix} \mathbf{1}_l & \mathbf{F} \end{bmatrix} \quad \text{and} \quad \mathbf{Q} = \begin{bmatrix} -\mathbf{F}^T & \mathbf{1}_n \end{bmatrix} \quad (20)$$

- Above equation tells us that the product of the $l \times b$ matrix \mathbf{B} and the $b \times n$ matrix \mathbf{Q}^T is the $l \times n$ zero matrix. In other words, the product of every row of \mathbf{B} and every column of \mathbf{Q}^T is zero.

Proof: For Eq. 19 i.e. $\mathbf{BQ}^T = \mathbf{0}$ and $\mathbf{QB}^T = \mathbf{0}$

- From $\mathbf{Bv} = \mathbf{0}$ and $\mathbf{v} = \mathbf{Q}^T \mathbf{e}$, we have

$$\mathbf{BQ}^T \mathbf{e} = \mathbf{0} \quad (21)$$

Proof: For Eq. 19 i.e. $\mathbf{BQ}^T = \mathbf{0}$ and $\mathbf{QB}^T = \mathbf{0}$

- From $\mathbf{Bv} = \mathbf{0}$ and $\mathbf{v} = \mathbf{Q}^T \mathbf{e}$, we have

$$\mathbf{BQ}^T \mathbf{e} = \mathbf{0} \quad (21)$$

- Above means that whenever we multiply any n -vector \mathbf{e} by \mathbf{BQ}^T , we get the zero vector. Therefore, Eq. 21 implies that the matrix \mathbf{BQ}^T has all its elements equal to zero.

Proof: For Eq. 19 i.e. $\mathbf{BQ}^T = \mathbf{0}$ and $\mathbf{QB}^T = \mathbf{0}$

- From $\mathbf{Bv} = \mathbf{0}$ and $\mathbf{v} = \mathbf{Q}^T \mathbf{e}$, we have

$$\mathbf{BQ}^T \mathbf{e} = \mathbf{0} \quad (21)$$

- Above means that whenever we multiply any n -vector \mathbf{e} by \mathbf{BQ}^T , we get the zero vector. Therefore, Eq. 21 implies that the matrix \mathbf{BQ}^T has all its elements equal to zero.
- Therefore, we establish $\mathbf{BQ}^T = \mathbf{0}$ and $\mathbf{QB}^T = \mathbf{0}$

Proof: For Eq. 20 i.e. $\mathbf{B} = \begin{bmatrix} \mathbf{1}_l & \mathbf{F} \end{bmatrix}$ and $\mathbf{Q} = \begin{bmatrix} -\mathbf{F}^T & \mathbf{1}_n \end{bmatrix}$

- From eq. 12, \mathbf{Q} was of the form

$$\mathbf{Q} = \begin{bmatrix} \mathbf{E} & \mathbf{I}_n \end{bmatrix}$$

Proof: For Eq. 20 i.e. $\mathbf{B} = \begin{bmatrix} \mathbf{1}_l & \mathbf{F} \end{bmatrix}$ and $\mathbf{Q} = \begin{bmatrix} -\mathbf{F}^T & \mathbf{1}_n \end{bmatrix}$

- From eq. 12, \mathbf{Q} was of the form

$$\mathbf{Q} = \begin{bmatrix} \mathbf{E} & \mathbf{I}_n \end{bmatrix}$$

- So,

$$\mathbf{BQ}^T = [\mathbf{I}_l | \mathbf{F}] \begin{bmatrix} \mathbf{E}^T \\ \mathbf{I}_n \end{bmatrix}$$

Proof: For Eq. 20 i.e. $\mathbf{B} = [\mathbf{I}_l \quad \mathbf{F}]$ and $\mathbf{Q} = [\mathbf{-F}^T \quad \mathbf{I}_n]$

- From eq. 12, \mathbf{Q} was of the form

$$\mathbf{Q} = [\mathbf{E} \quad \mathbf{I}_n]$$

- So,

$$\mathbf{BQ}^T = [\mathbf{I}_l | \mathbf{F}] \begin{bmatrix} \mathbf{E}^T \\ \mathbf{I}_n \end{bmatrix}$$

- Noting that \mathbf{I}_l has the same number of columns as \mathbf{E}^T has rows, we conclude that

$$\mathbf{BQ}^T = \mathbf{I}_l \mathbf{E}^T + \mathbf{F} \mathbf{I}_n = \mathbf{E}^T + \mathbf{F} = \mathbf{0}$$

Proof: For Eq. 20 i.e. $\mathbf{B} = [\mathbf{I}_l \quad \mathbf{F}]$ and $\mathbf{Q} = [\mathbf{-F}^T \quad \mathbf{I}_n]$

- From eq. 12, \mathbf{Q} was of the form

$$\mathbf{Q} = [\mathbf{E} \quad \mathbf{I}_n]$$

- So,

$$\mathbf{BQ}^T = [\mathbf{I}_l | \mathbf{F}] \begin{bmatrix} \mathbf{E}^T \\ \mathbf{I}_n \end{bmatrix}$$

- Noting that \mathbf{I}_l has the same number of columns as \mathbf{E}^T has rows, we conclude that

$$\mathbf{BQ}^T = \mathbf{I}_l \mathbf{E}^T + \mathbf{F} \mathbf{I}_n = \mathbf{E}^T + \mathbf{F} = \mathbf{0}$$

- Hence, $\mathbf{E}^T = -\mathbf{F}$ and transposing, $\mathbf{E} = -\mathbf{F}^T$

Proof: For Eq. 20 i.e. $\mathbf{B} = [\mathbf{I}_l \quad \mathbf{F}]$ and $\mathbf{Q} = [\mathbf{-F}^T \quad \mathbf{I}_n]$

- From eq. 12, \mathbf{Q} was of the form

$$\mathbf{Q} = [\mathbf{E} \quad \mathbf{I}_n]$$

- So,

$$\mathbf{BQ}^T = [\mathbf{I}_l | \mathbf{F}] \begin{bmatrix} \mathbf{E}^T \\ \mathbf{I}_n \end{bmatrix}$$

- Noting that \mathbf{I}_l has the same number of columns as \mathbf{E}^T has rows, we conclude that

$$\mathbf{BQ}^T = \mathbf{I}_l \mathbf{E}^T + \mathbf{F} \mathbf{I}_n = \mathbf{E}^T + \mathbf{F} = \mathbf{0}$$

- Hence, $\mathbf{E}^T = -\mathbf{F}$ and transposing, $\mathbf{E} = -\mathbf{F}^T$
- Using this conclusion into eq. 12, we see that

$$\mathbf{Q} = [\mathbf{-F}^T \quad \mathbf{I}_n]$$

- **Summary for Loop set Analysis** KVL is expressed by $\mathbf{B}\mathbf{v} = \mathbf{0}$, and KCL by $\mathbf{j} = \mathbf{B}^T \mathbf{i}$ where \mathbf{i} is the loop current vector. As a result of our choice of reference directions, the fundamental loop matrix \mathbf{B} is of the form (2). These equations are valid irrespective of the nature of the branches.

- **Summary for Loop set Analysis** KVL is expressed by $\mathbf{B}\mathbf{v} = \mathbf{0}$, and KCL by $\mathbf{j} = \mathbf{B}^T \mathbf{i}$ where \mathbf{i} is the loop current vector. As a result of our choice of reference directions, the fundamental loop matrix \mathbf{B} is of the form (2). These equations are valid irrespective of the nature of the branches.
- **Summary for Cut set Analysis** KCL requires that $\mathbf{Q}\mathbf{j} = \mathbf{0}$. KVL is expressed by $\mathbf{v} = \mathbf{Q}^T \mathbf{e}$. As a result of our numbering convention, the fundamental cut-set matrix \mathbf{Q} is of the form of (12). These equations are valid irrespective of the nature of the branches.

Practice

(1) Consider the graph \mathcal{G} of below Figure. List all the fundamental loops and all the fundamental cut sets corresponding to tree T_1 shown in Fig. 2.

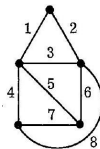


Figure 17: Planar graph
